



Computer Science Department



Cairo University

CS504

Digital Logic & Computer Organization

Lecture 7


Lecture Outline (Chapter 4)

- ★ **Combinational Circuits (Section 4.2)**
- ★ **Analysis Procedure (Section 4.3)**
- ★ **Design Procedure (Section 4.4)**
 - **BCD-to-Excess-3 Converter**
 - **Seven-Segment Decoder**
- ★ **Binary Adder (Section 4.5)**
 - **Half-Adder**
 - **Full Adder**
 - **Carry Propagate Adder**
 - **Carry Propagation**
 - **Carry Look-Ahead Generator**
 - **4-bit Carry Look-Ahead Adder (CLAA)**

Combinational Circuits

★ Output is function of input only

i.e. no feedback

 


When **input** changes, **output** may change (after a delay)

Combinational Circuits (2)


★ Analysis

 - Given a circuit, find out its *function*
- Function may be expressed as:
 - ◆ Boolean function
 - ◆ Truth table




★ Design

 - Given a desired function, determine its *circuit*
- Function may be expressed as:
 - ◆ Boolean function
 - ◆ Truth table



Analysis Procedure

★ Boolean Expression Approach

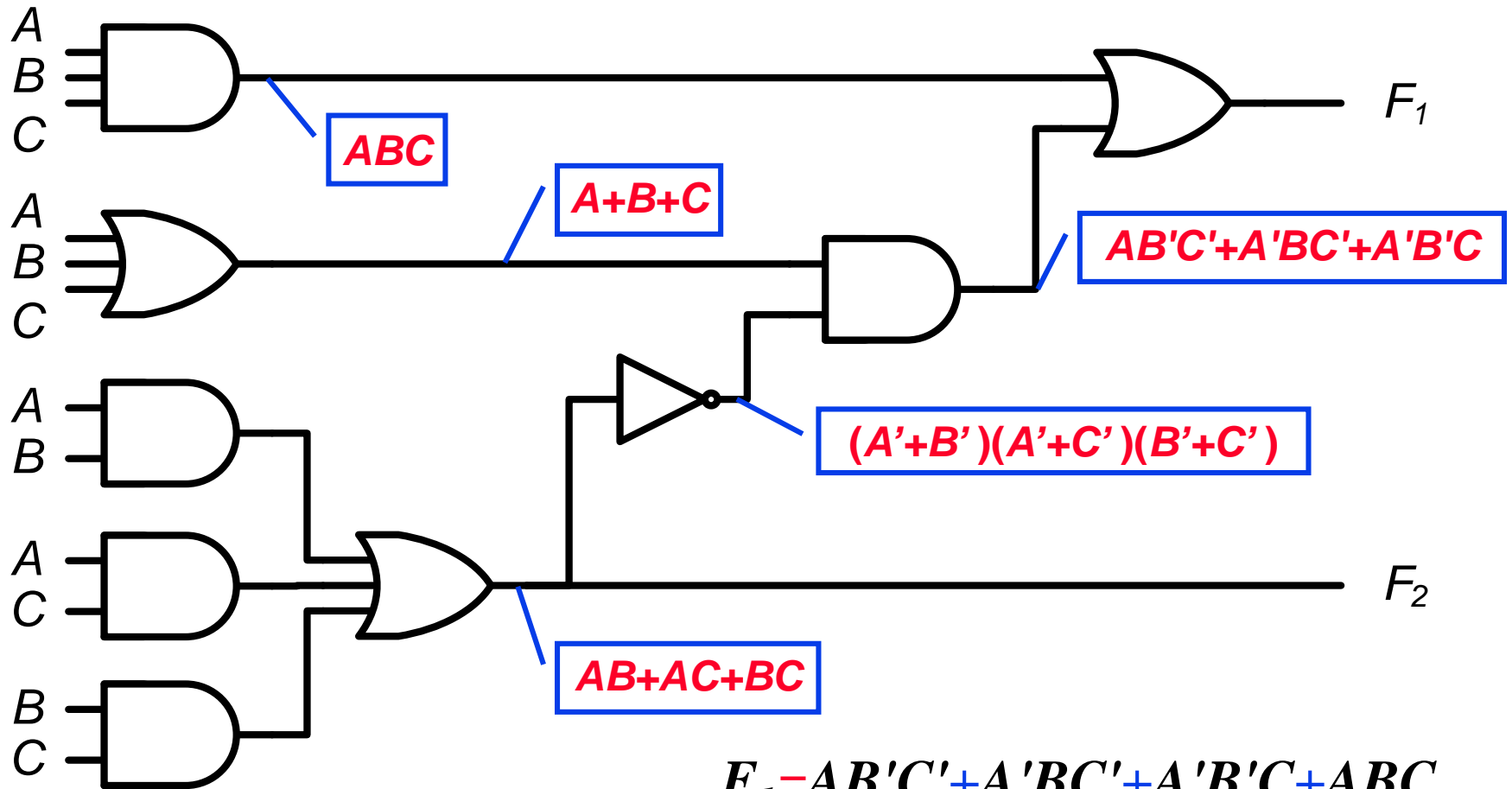


$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure (2)


★ Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0

Analysis Procedure (3)


★ Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0

Analysis Procedure (4)


★ Truth Table Approach

 

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0

Analysis Procedure (5)


★ Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

Analysis Procedure (6)


★ Truth Table Approach

 

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

Analysis Procedure (7)


★ Truth Table Approach

 

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1

Analysis Procedure (8)


★ Truth Table Approach

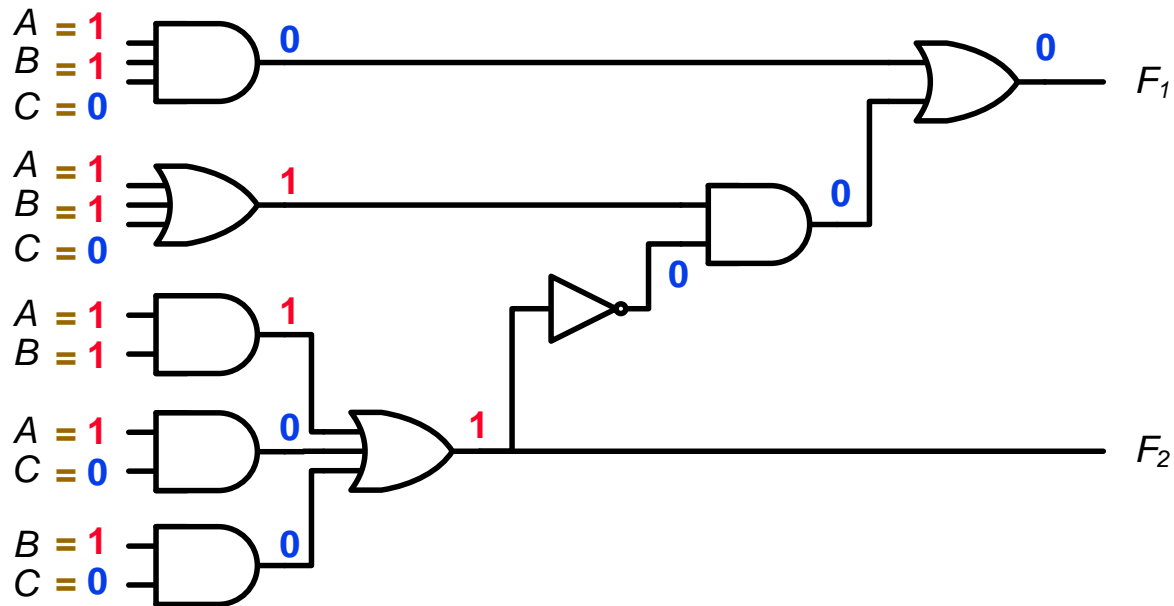

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1

Analysis Procedure (9)

★ Truth Table Approach

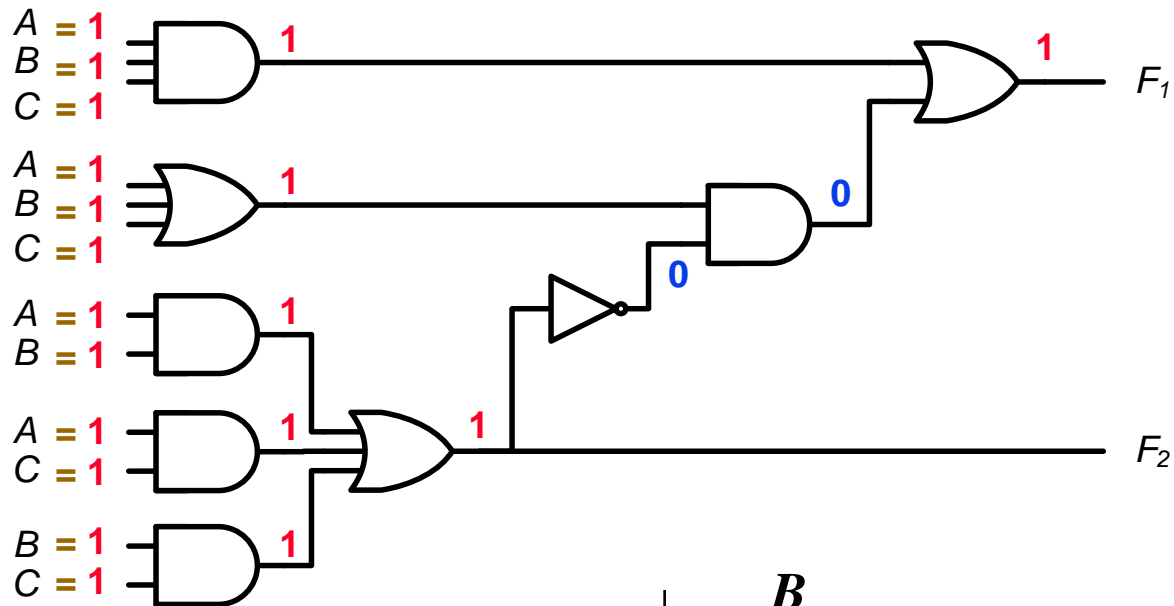

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

	B			
	0	1	0	1
A	1	0	1	0
	C			

	B			
	0	0	1	0
A	0	1	1	1
	C			

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$


Design Procedure

★ Given a problem statement:

- Determine the number of *inputs* and *outputs*
- Derive the truth table
- Simplify the Boolean expression for each output
- Produce the required circuit

 Example:


Design a circuit to convert a “BCD” code to “Excess 3” code




Design Procedure (2)

★ BCD-to-Excess-3 Converter


<i>A B C D</i>	<i>w x y z</i>
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

 


$$w = A + BC + BD$$

 

$$x = B'C + B'D + BC'D'$$

 

$$y = C'D' + CD$$

 

$$z = D'$$

Design Procedure (3)

★ The simplified functions in SOP form

$$z = D'$$

This two-level implementation requires 7 AND gates, 3 OR gates and 3 inverter gates for variables *B*, *C*, and *D*.

$$y = CD + C'D'$$

$$x = B'C + B'D + BC'D'$$

$$w = A + BC + BD$$

★ Another implementation by algebraic manipulation

$$z = D'$$

This three-level implementation requires 4 AND gates, 4 OR gates and 3 inverter gates for variables *B*, *D* and the sum term $(C+D)$. (Better)

$$y = CD + C'D' = CD + (C+D)'$$


$$x = B'C + B'D + BC'D' = B'(C+D) + B(C+D)'$$

$$w = A + BC + BD = A + B(C+D)$$

Design Procedure (4)

★ BCD-to-Excess-3 Converter

<i>A B C D</i>	<i>w x y z</i>
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

 

$$w = A + B(C + D)$$

$$y = (C + D)' + CD$$




$$x = B'(C + D) + B(C + D)'$$

$$z = D'$$

Design Procedure (5)

★ Seven-Segment Decoder

<i>w x y z</i>	<i>a b c d e f g</i>
0 0 0 0	1 1 1 1 1 1 0
0 0 0 1	0 1 1 0 0 0 0
0 0 1 0	1 1 0 1 1 0 1
0 0 1 1	1 1 1 1 0 0 1
0 1 0 0	0 1 1 0 0 1 1
0 1 0 1	1 0 1 1 0 1 1
0 1 1 0	1 0 1 1 1 1 1
0 1 1 1	1 1 1 0 0 0 0
1 0 0 0	1 1 1 1 1 1 1
1 0 0 1	1 1 1 1 0 1 1
1 0 1 0	x x x x x x x
1 0 1 1	x x x x x x x
1 1 0 0	x x x x x x x
1 1 0 1	x x x x x x x
1 1 1 0	x x x x x x x
1 1 1 1	x x x x x x x

   

$$a = w + y + xz + x'z'$$

$$b = \dots$$

$$c = \dots$$


$$d = \dots$$

Binary Adder


★ Half Adder

- Adds **1-bit** plus **1-bit**
- Produces **Sum** and **Carry**

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

 
$$\begin{array}{r} x \\ + y \\ \hline C \quad S \end{array}$$



Binary Adder (2)

★ Full Adder

 - Adds **1-bit** plus **1-bit** plus **1-bit**
- Produces **Sum** and **Carry**



x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

			y
	0	1	0
x	1	0	1
			z

$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

			y
	0	0	1
x	0	1	1
			z

$$C = xy + xz + yz$$



$$\begin{array}{r} x \\ + y \\ + z \\ \hline C \quad S \end{array}$$

Binary Adder (3)

★ Full Adder



$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

 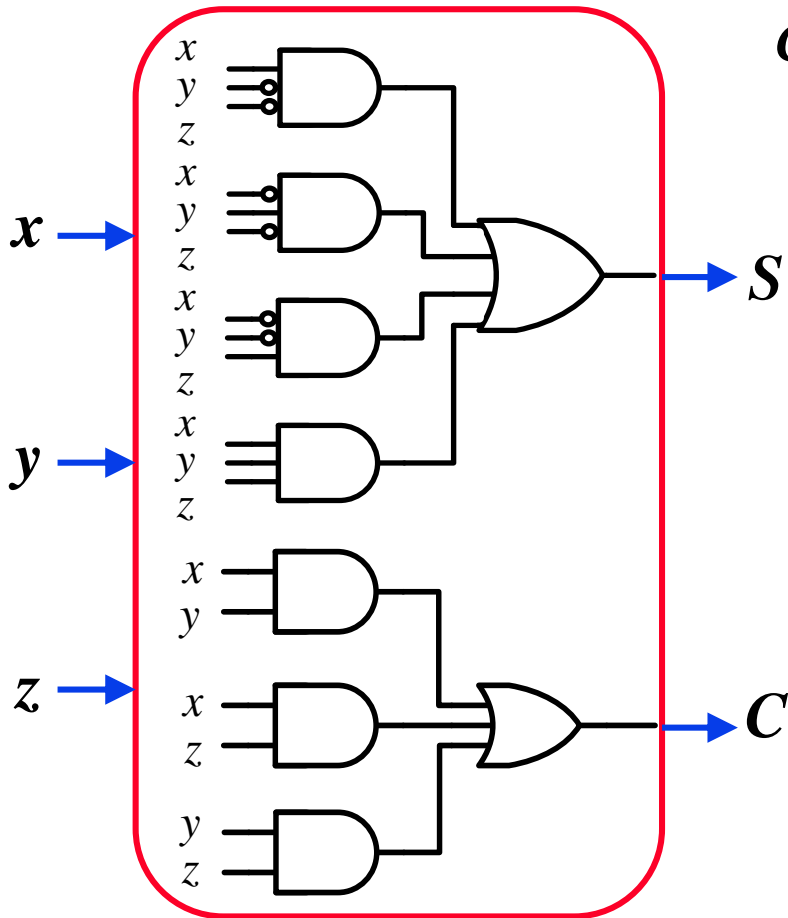

Binary Adder (4)

★ Full Adder

  

Binary Adder (5)

★ Full Adder


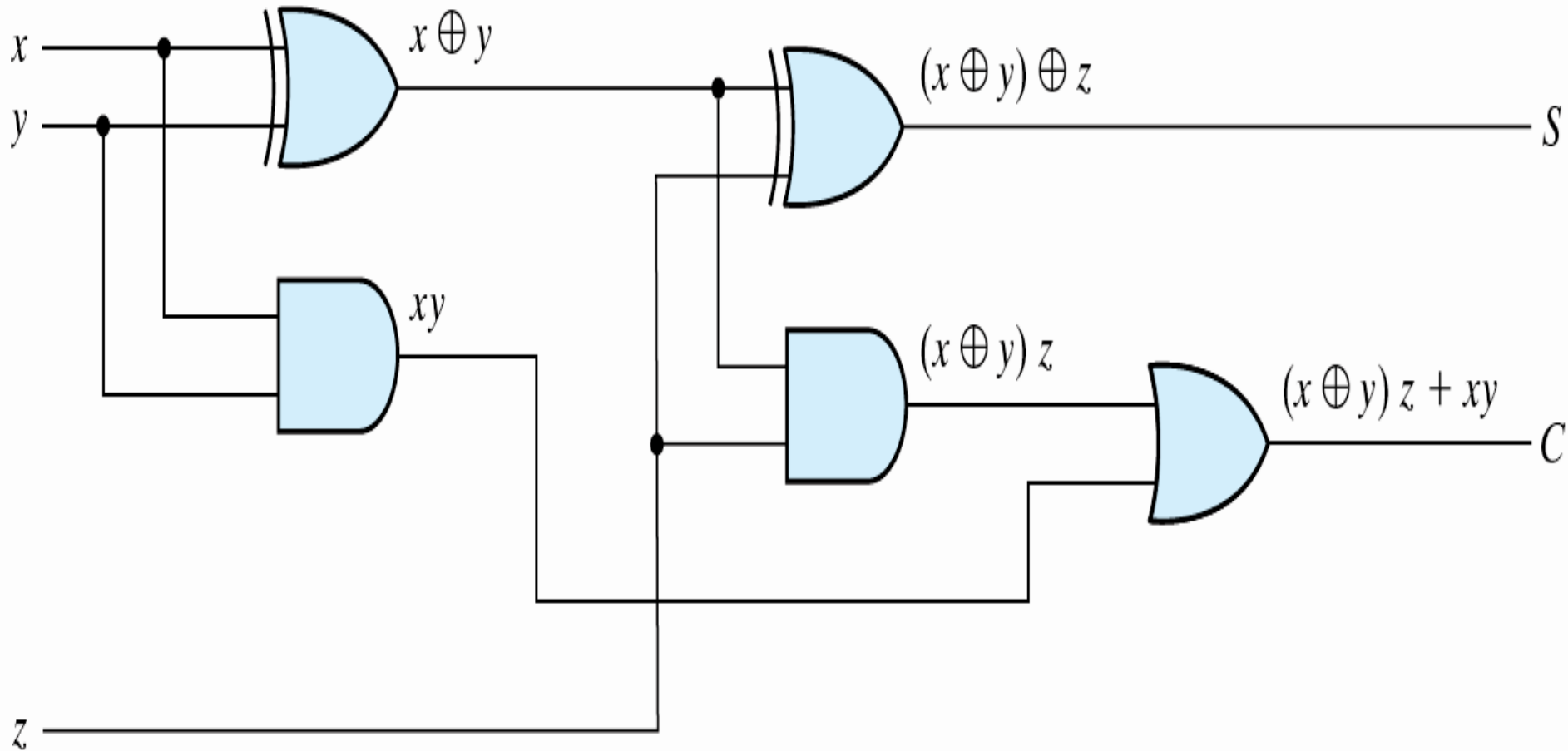


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

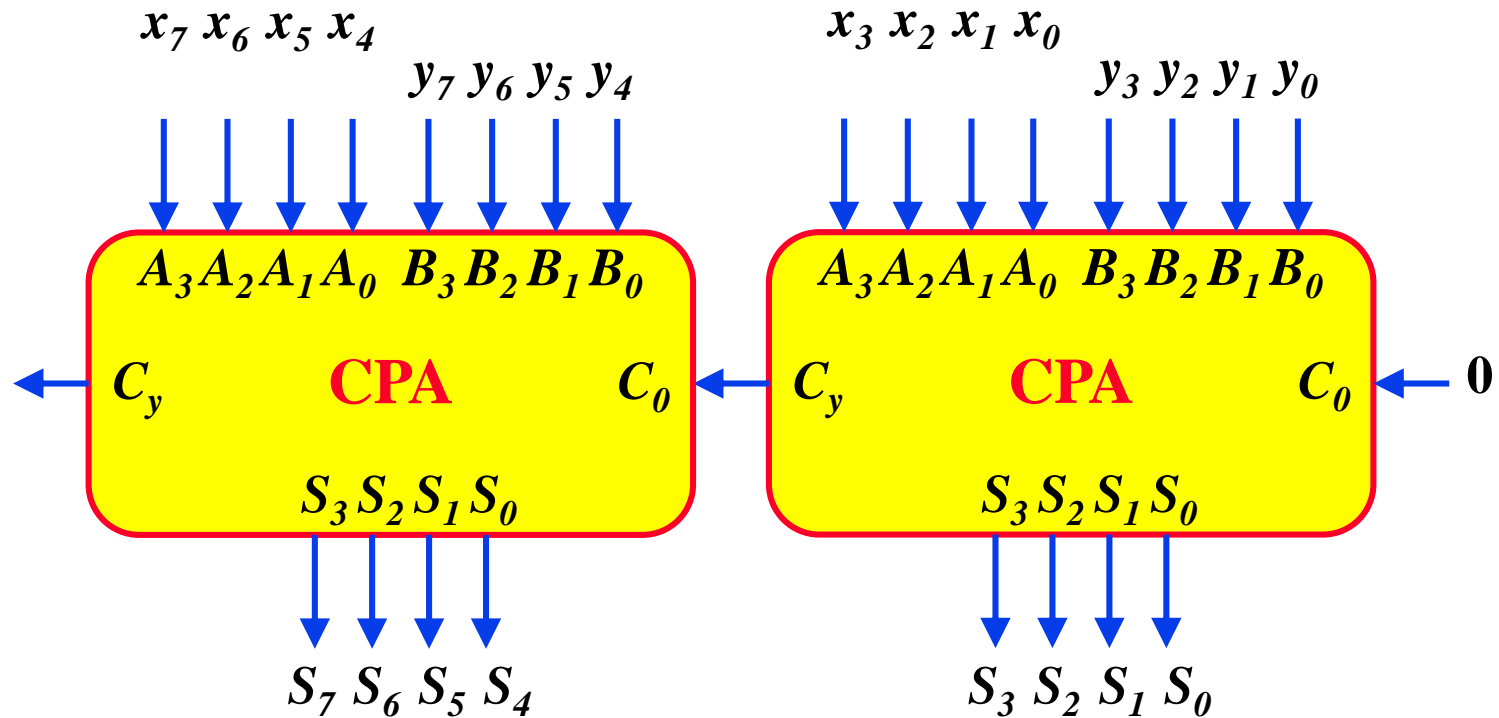

Binary Adder (7)


★ Carry Propagate Adder



Carry Propagation

- ★ This is also called **Ripple Carry Adder (RCA)**, because of the construction with full adders are connected in cascade.
- ★ This causes a unstable factor on carry bit, and produces a longest propagation delay.
- ★ The signal from C_i to the output carry C_{i+1} , propagates through an AND and OR gates, so, for an n-bit RCA, there are $2n$ gate levels for the carry to propagate from input to output.
- ★ Because the propagation delay will affect the output signals on different time, so the signals are given enough time to get the precise and stable outputs.
- ★ The most widely used technique employs the principle of **carry look-ahead** to improve the speed of the algorithm.

Carry Look-Ahead Generator

 

$P_i = A_i \oplus B_i$ steady state value

$G_i = A_i B_i$ steady state value

G_i : **Carry Generate** because it produces a carry regardless of the input carry C_i

P_i : **Carry Propagate** because it determines whether a carry into a stage i will propagate into a stage $i+1$

Output sum and carry

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

$$C_0 = \text{input carry}$$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

★ C_3 does not have to wait for C_2 and C_1 to propagate.

Carry Look-Ahead Generator (2)

★ C_3 is propagated at the same time as C_2 and C_1 .

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

4-bit Carry Look-Ahead Adder (CLAA)

★ Delay time of n-bit CLAA = XOR + (AND + OR) + XOR

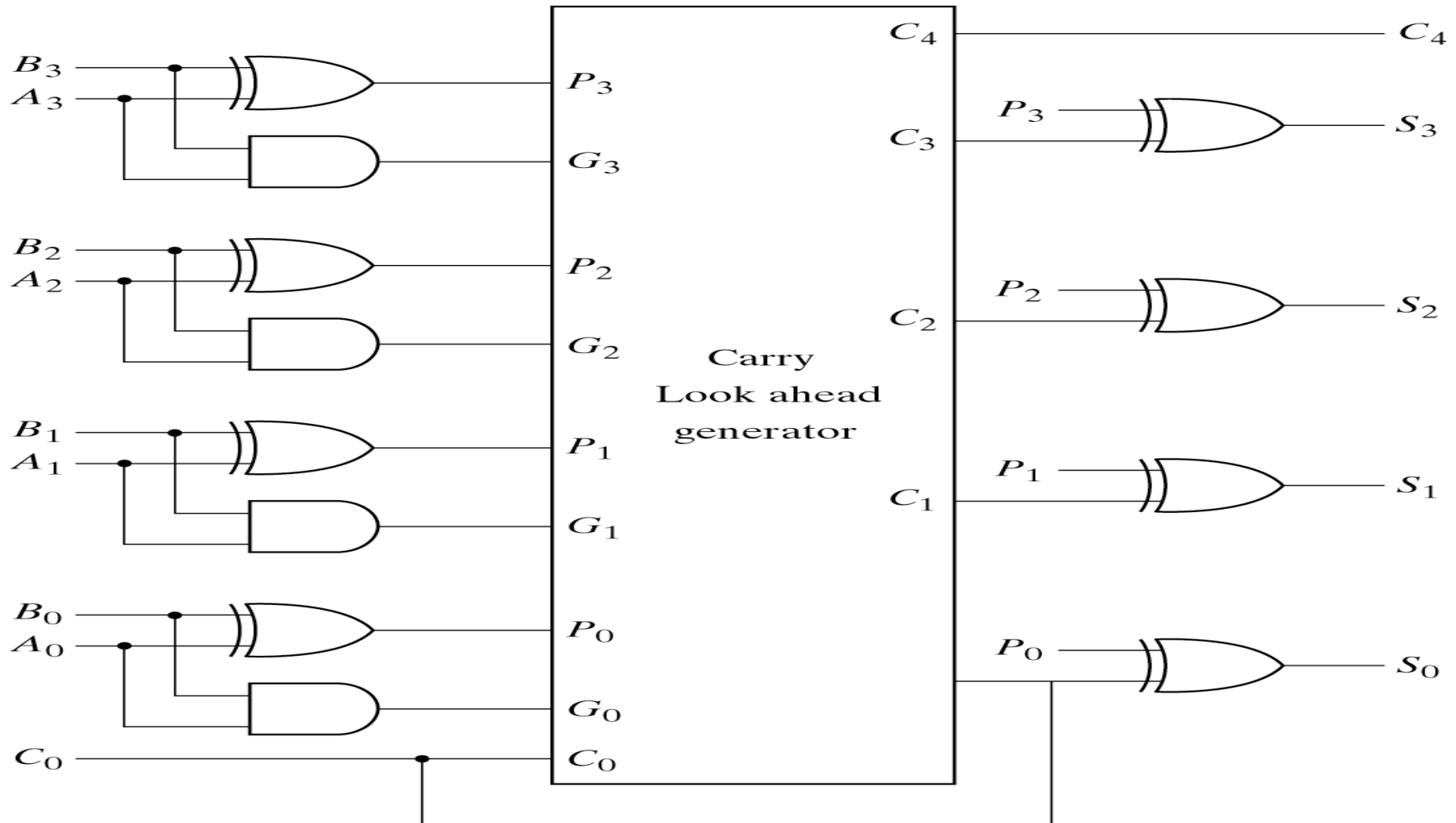


Fig. 4-12 4-Bit Adder with Carry Lookahead

The End

Questions?