



# Computer Science Department

---



Cairo University

## CS504

# Digital Logic & Computer Organization

## Lecture 4

# Lecture Outline (Chapter 3)

---

## ★ Circuit Optimization (Section 3.1)

- Literal Cost
- Gate Input Cost
- Boolean Function Optimization

## ★ Karnaugh Map (K-Map) (Section 3.2)

- Two-Variable K-Map
- Three-Variable K-Map

## ★ Four-Variable K-Map (Section 3.3)

## ★ Product-Of-Sums (POS) Simplification (Section 3.4)

# Circuit Optimization

---

- **Goal: To obtain the simplest implementation for a given function**
- **Optimization is a more formal approach to simplification that is performed using a specific procedure or algorithm**
- **Optimization requires a cost criterion to measure the simplicity of a circuit**
- **Distinct cost criteria we will use:**
  - Literal cost (L)
  - Gate input cost (G)
  - Gate input cost including inverters (GN)

# Literal Cost

---

- **Literal** – a variable or its complement
- **Literal cost** – the number of literal appearances in a Boolean expression corresponding to the logic circuit diagram
- **Example: Boolean expressions for F**
  - $F = B D + A \bar{B} C + A \bar{C} \bar{D}$  **L = 8**
  - $F = B D + A \bar{B} C + A \bar{B} \bar{D} + A B \bar{C}$  **L = 11**
  - $F = (A+B)(A+D)(B+C+\bar{D})(\bar{B}+\bar{C}+D)$  **L = 10**
  - Which solution is best? **First solution is best**

# Gate Input Cost

- **Gate Input Cost:** Count of total number of inputs to the gates in the logic circuit implementation

- Two gate input costs are defined:

**G = Count of gate inputs without counting Inverters**

**GN = Count of gate inputs + count of Inverters**

- For SOP and POS equations, the gate input cost can be found from the Boolean expression by finding the sum of:

- All literal appearances
- Number of terms excluding single literal terms (added to G)
- Number of distinct complemented single literals (added to GN)

- **Example:**

- $F = B D + A \overline{B} C + A \overline{C} \overline{D}$

$$L = 8 \quad G = L + 3 = 11$$

$$GN = G + 3 = 14$$

# Cost Criteria (continued)


- Example 1:

- $F = A + \underset{\text{blue square}}{B} \underset{\text{blue square}}{C} + \overset{\text{red triangle}}{\bar{B}} \overset{\text{red triangle}}{\bar{C}}$

$$GN = \text{blue G} + \text{red 2} = 9$$

$$L = 5$$

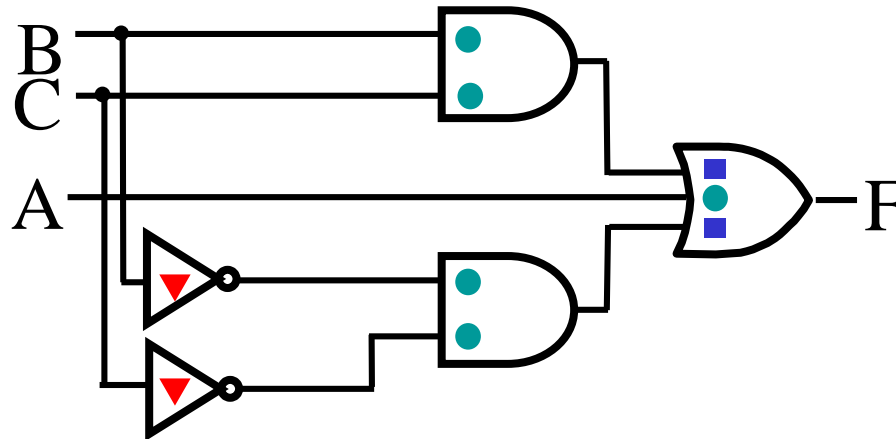
$$G = \text{teal L} + \text{blue 2} = 7$$



- L (literal count) counts the AND inputs and the single literal OR input.
- G (gate input count) adds the remaining OR gate inputs
- GN(gate input count with NOTs) adds the inverter inputs

# Cost Criteria (continued)

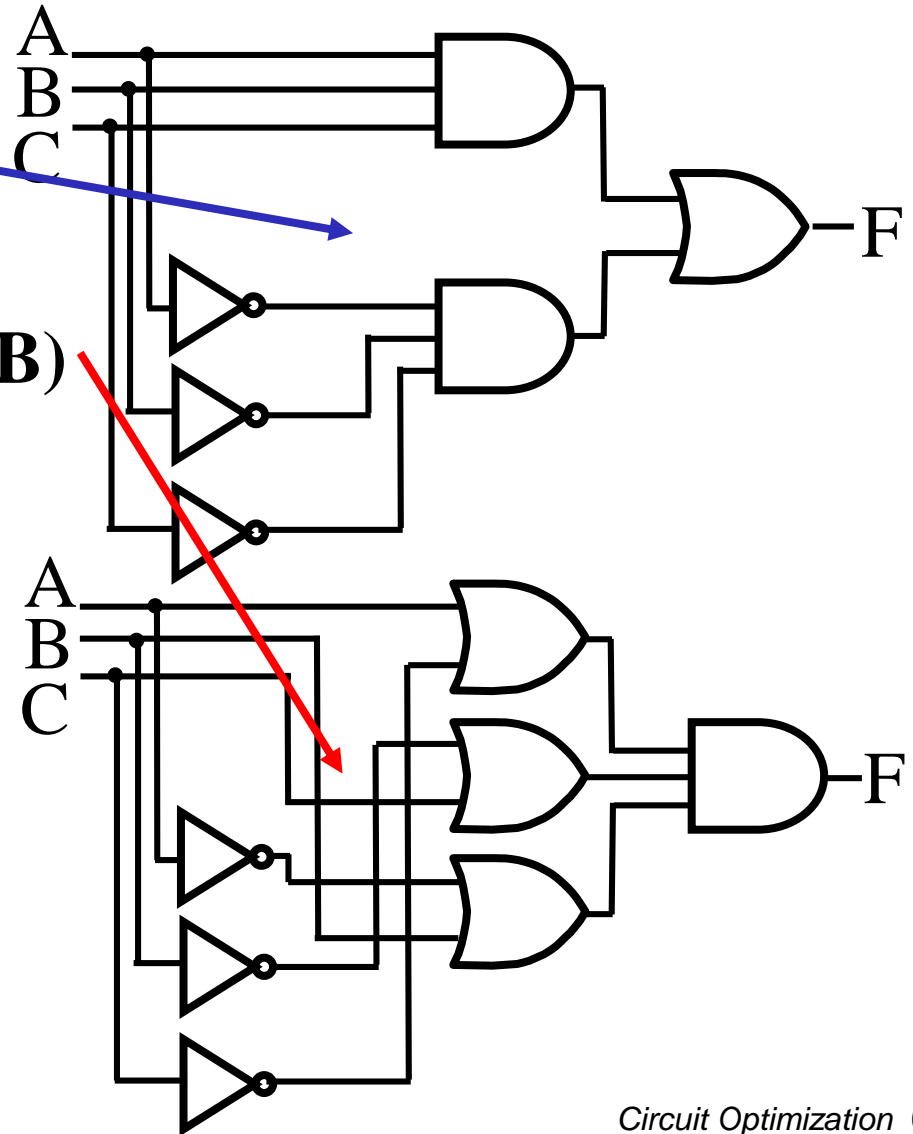- **Example 2:**
- $F = A B C + \bar{A} \bar{B} \bar{C}$   
 $L = 6 \quad G = 8 \quad GN = 11$
- $F = (A + \bar{C})(\bar{B} + C)(\bar{A} + B)$   
 $L = 6 \quad G = 9 \quad GN = 12$
- Same function and same literal cost
- But first circuit has better gate input count and better gate input count with NOTs
- Select first circuit!



# Cost Criteria Summary

---

- Literal Count:
  - Simple to evaluate by counting all literals
  - However, does not represent circuit complexity accurately in all cases
- Gate Input Cost (or Count):
  - Good measure of logic implementation
  - Proportional to the number of transistors and wires used in the implementation
  - Important when measuring cost of circuits with more than two levels



# Boolean Function Optimization

---

- **Minimizing the gate input (or literal) cost of a Boolean equation reduces the circuit cost**
- **We choose gate input cost**
- **Boolean Algebra and graphical techniques are tools to minimize cost criteria values**
- **Some important questions:**
  - **When do we stop trying to reduce the cost?**
  - **Do we know when we have a minimum cost?**
- **Treat optimum or near-optimum cost functions for two-level (SOP and POS) circuits first**
- **Introduce a graphical technique using Karnaugh maps (K-maps for short)**

# Karnaugh Map (K-map)

---

- **A K-map is a collection of squares**
  - **Each square represents a minterm**
  - **The collection of squares is a graphical representation of a Boolean function**
  - **Adjacent squares differ in the value of one variable**
  - **Alternative algebraic expressions for the same function are derived by recognizing patterns of squares**
- **The K-map can be viewed as**
  - **A reorganized version of the truth table**

# Some Uses of K-Maps

---

- **Provide a means for:**
  - **Finding optimum or near optimum**
    - **SOP and POS standard forms**
    - **Two-level AND/OR and OR/AND circuits**
- for functions with small numbers of variables**
- **Visualizing concepts related to manipulating Boolean expressions, and**
- **Demonstrating concepts used by computer-aided design programs to simplify large circuits**

# Two-Variable K-Map

---

- A 2-variable Karnaugh Map:
  - Minterm  $m_0$  and minterm  $m_1$  are “adjacent” they differ in the value of variable  $y$
  - Similarly, minterm  $m_0$  and minterm  $m_2$  are adjacent and differ in  $x$
  - Also,  $m_1$  and  $m_3$  differ in the  $x$  variable
  - Finally,  $m_2$  and  $m_3$  differ in the  $y$  variable

$x \backslash y$	$y = 0$	$y = 1$
$x = 0$	$m_0 = \bar{x} \bar{y}$	$m_1 = \bar{x} y$
$x = 1$	$m_2 = x \bar{y}$	$m_3 = x y$

# K-Map and Truth Tables

---

- The K-Map is a different form of the truth table

**Truth Table**

<b>Input Values (x,y)</b>	<b>Function Value F(x,y)</b>
<b>0 0</b>	<b>1</b>
<b>0 1</b>	<b>0</b>
<b>1 0</b>	<b>1</b>
<b>1 1</b>	<b>1</b>

**K-Map**

<b>x \ y</b>	<b>y = 0</b>	<b>y = 1</b>
<b>x = 0</b>	<b>1</b>	<b>0</b>
<b>x = 1</b>	<b>1</b>	<b>1</b>

# K-Map Function Minimization

- $F(x,y) = m_0 + m_2 + m_3$

$$F = \bar{x} \bar{y} + x \bar{y} + x y$$

- Two adjacent cells containing 1's can be combined using the Minimization Theorem

**K-Map**

$x \backslash y$	$y = 0$	$y = 1$
$x = 0$	1	0
$x = 1$	1	1

- $m_0 + m_2 = \bar{x} \bar{y} + x \bar{y} = (\bar{x} + x) \bar{y} = \bar{y}$
- $m_2 + m_3 = x \bar{y} + x y = x (\bar{y} + y) = x$
- Therefore, F can be simplified as  $F = x + \bar{y}$

# Three Variable K-Map

$x \backslash yz$	$yz=00$	$yz=01$	$yz=11$	$yz=10$
$x=0$	$m_0$	$m_1$	$m_3$	$m_2$
$x=1$	$m_4$	$m_5$	$m_7$	$m_6$

- Where each minterm corresponds to the product terms:

$x \backslash yz$	$yz=00$	$yz=01$	$yz=11$	$yz=10$
$x=0$	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
$x=1$	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

- Note that if the binary value for an index differs in one bit position, the minterms are adjacent on the K-Map

# Alternative K-Map Labeling

- **K-Map largely involves:**
  - Entering values into the map, and
  - Reading off product terms from the map
- **Alternate labelings are useful:**

		$y \quad z$			
		00	01	$\overbrace{11 \quad 10}^y$	
$x$	0	0	1	3	2
	1	4	5	7	6
		$\underbrace{\hspace{10em}}_z$			

		$\bar{y}$		$y$	
$\bar{x}$	0	1	3	2	
$x$	4	5	7	6	
		$\bar{z}$	$z$	$\bar{z}$	



# Example Functions

- By convention, we represent the minterms of  $F$  by a '1' in the map and leave the entries that contain '0' blank
- Example 1:

$$F(x, y, z) = \sum(2, 3, 4, 5)$$

			<b>y</b>	
	0	1	3 <b>1</b>	2 <b>1</b>
<b>x</b>	4 <b>1</b>	5 <b>1</b>	7	6
			<b>z</b>	

- Example 2:

$$G(x, y, z) = \sum(3, 4, 6, 7)$$

- Learn the locations of the 8 indices based on the variable order shown

			<b>y</b>	
	0	1	3 <b>1</b>	2
<b>x</b>	4 <b>1</b>	5	7 <b>1</b>	6 <b>1</b>
			<b>z</b>	

# Combining Squares

---

- **By combining squares, we reduce number of literals in a product term, thereby reducing the gate input cost**
- **On a 3-variable K-Map:**
  - **One square represents a minterm with 3 variables**
  - **Two adjacent squares represent a term with 2 variables**
  - **Four adjacent squares represent a term with 1 variable**
  - **Eight adjacent square is the function 1 (no variables)**

# Example: Combining Squares

- Example:

$$F = \sum(2, 3, 6, 7)$$

			<b>y</b>	
	0	1	3 1	2 1
<b>x</b>	4	5	7 1	6 1
			<b>z</b>	


- Applying the Minimization Theorem 3 times:

$$\begin{aligned}
 F(x, y, z) &= \bar{x} y z + x y z + \bar{x} y \bar{z} + x y \bar{z} \\
 &= yz + y\bar{z} \\
 &= y
 \end{aligned}$$

- Thus the four terms that form a  $2 \times 2$  square correspond to the term 'y'.


# Combining Four Squares

- Example Shapes of 4-square Rectangles:

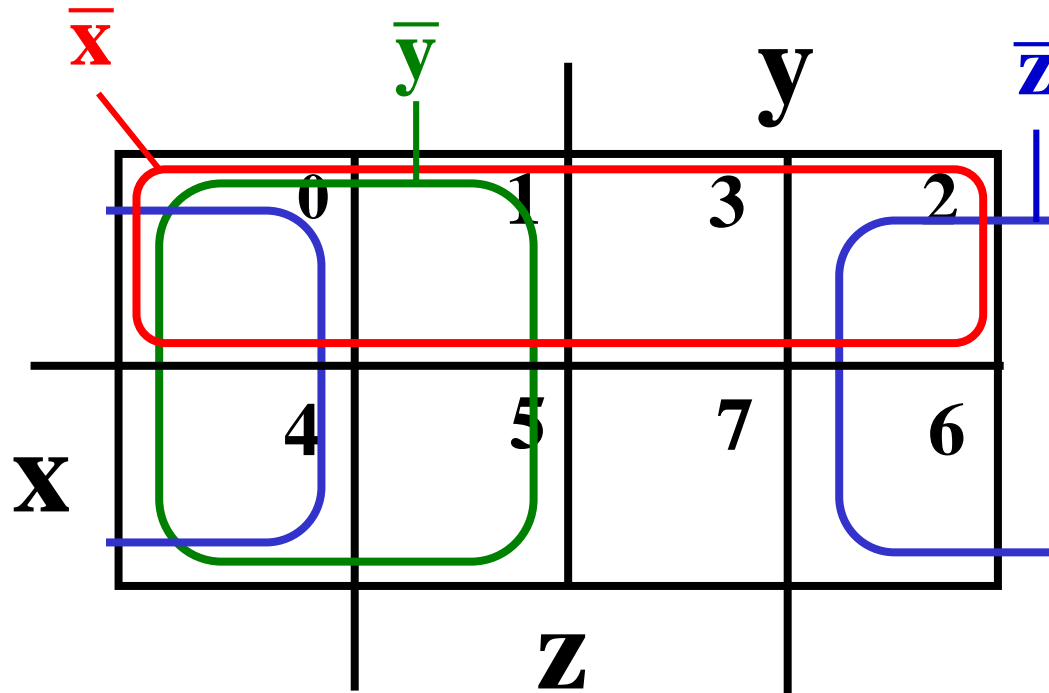

# Combining Two Squares


- Example Shapes of 2-square Rectangles:

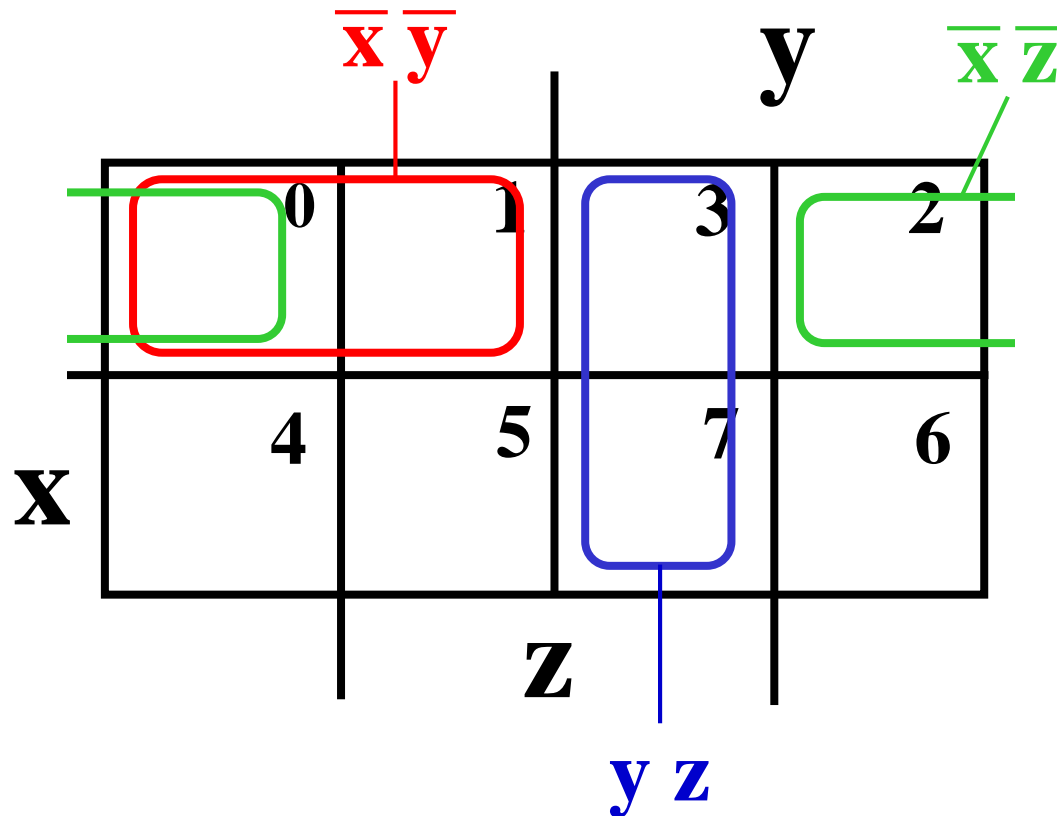

# Simplifying 3-Variable Functions

- K-Maps can be used to simplify Boolean functions
- Example: find an optimum SOP equation for

$$F(x, y, z) = \sum (0, 1, 2, 4, 6, 7)$$

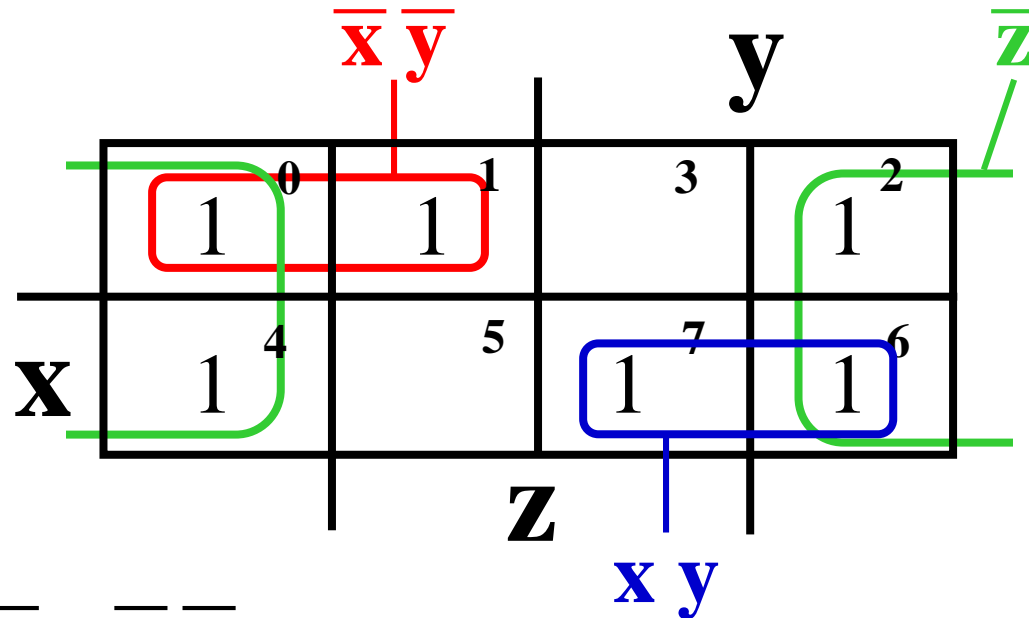

$$F = \bar{z} + \bar{x}\bar{y} + xy$$

# Four-Variable K-Map

		$\overline{Y}$		$Y$		
		$yz$				
		00	01	11	10	
$\overline{W}$	$WX$	$m_0 = \overline{w} \overline{x} \overline{y} \overline{z}$	$m_1 = \overline{w} \overline{x} \overline{y} z$	$m_3 = \overline{w} \overline{x} y z$	$m_2 = \overline{w} \overline{x} y \overline{z}$	$\overline{X}$
	01	$m_4 = \overline{w} x \overline{y} \overline{z}$	$m_5 = \overline{w} x \overline{y} z$	$m_7 = \overline{w} x y z$	$m_6 = \overline{w} x y \overline{z}$	
	11	$m_{12} = w x \overline{y} \overline{z}$	$m_{13} = w x \overline{y} z$	$m_{15} = w x y z$	$m_{14} = w x y \overline{z}$	$X$
	10	$m_8 = w \overline{x} \overline{y} \overline{z}$	$m_9 = w \overline{x} \overline{y} z$	$m_{11} = w \overline{x} y z$	$m_{10} = w \overline{x} y \overline{z}$	$\overline{X}$
		$\overline{Z}$	$Z$	$\overline{Z}$		

# 4-Variable K-map Terms


---

- **4-variable K-maps can have rectangles corresponding to:**
  - **Single square = 4-variable minterm**
  - **2 combined squares = 3-variable term**
  - **4 combined squares = 2-variable term**
  - **8 combined squares = 1 variable term**
  - **16 (all) combined squares = constant '1'**




# Combining Eight Squares

- Examples of 8-square Rectangles:

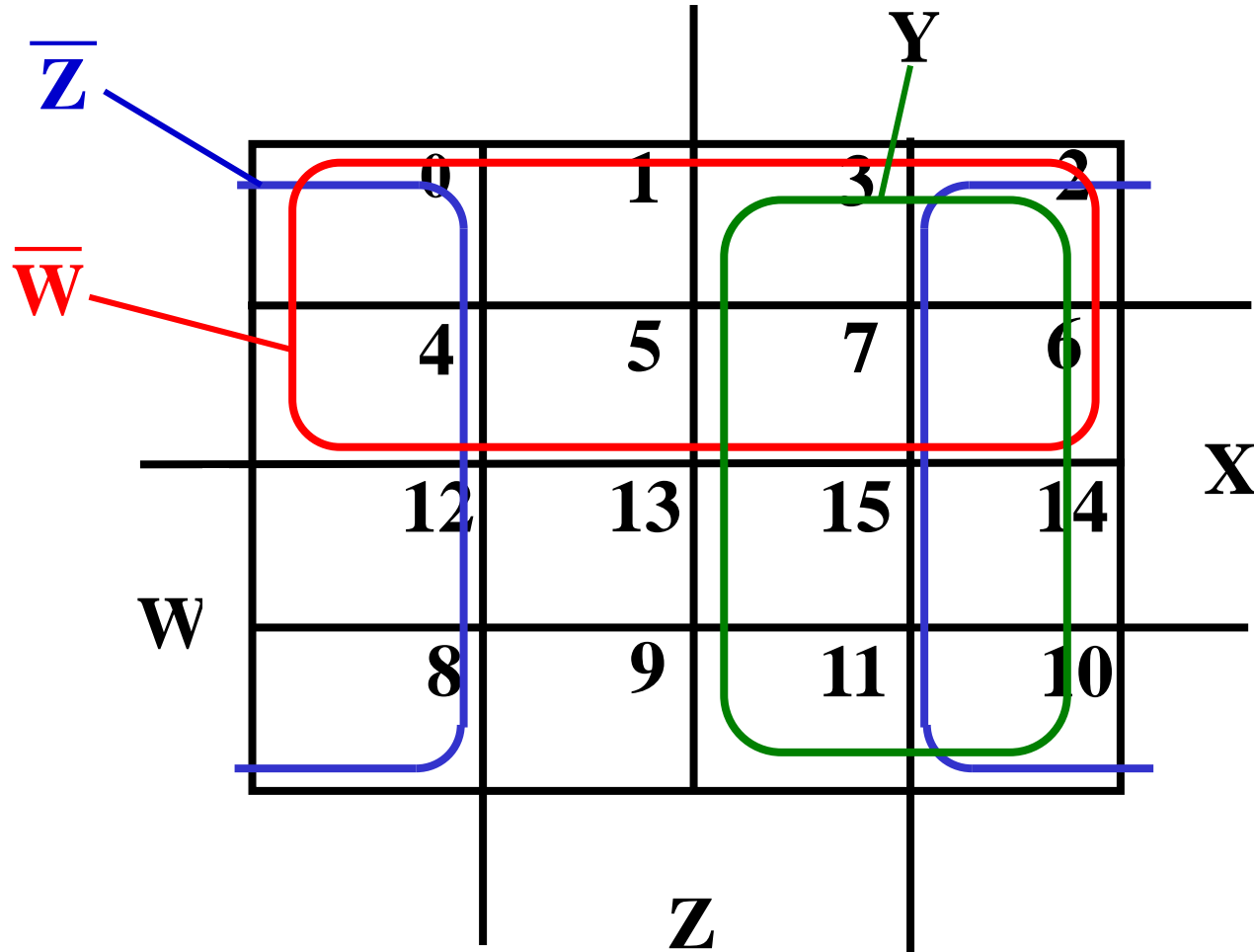


# Combining Four Squares

- Examples of 4-square Rectangles:

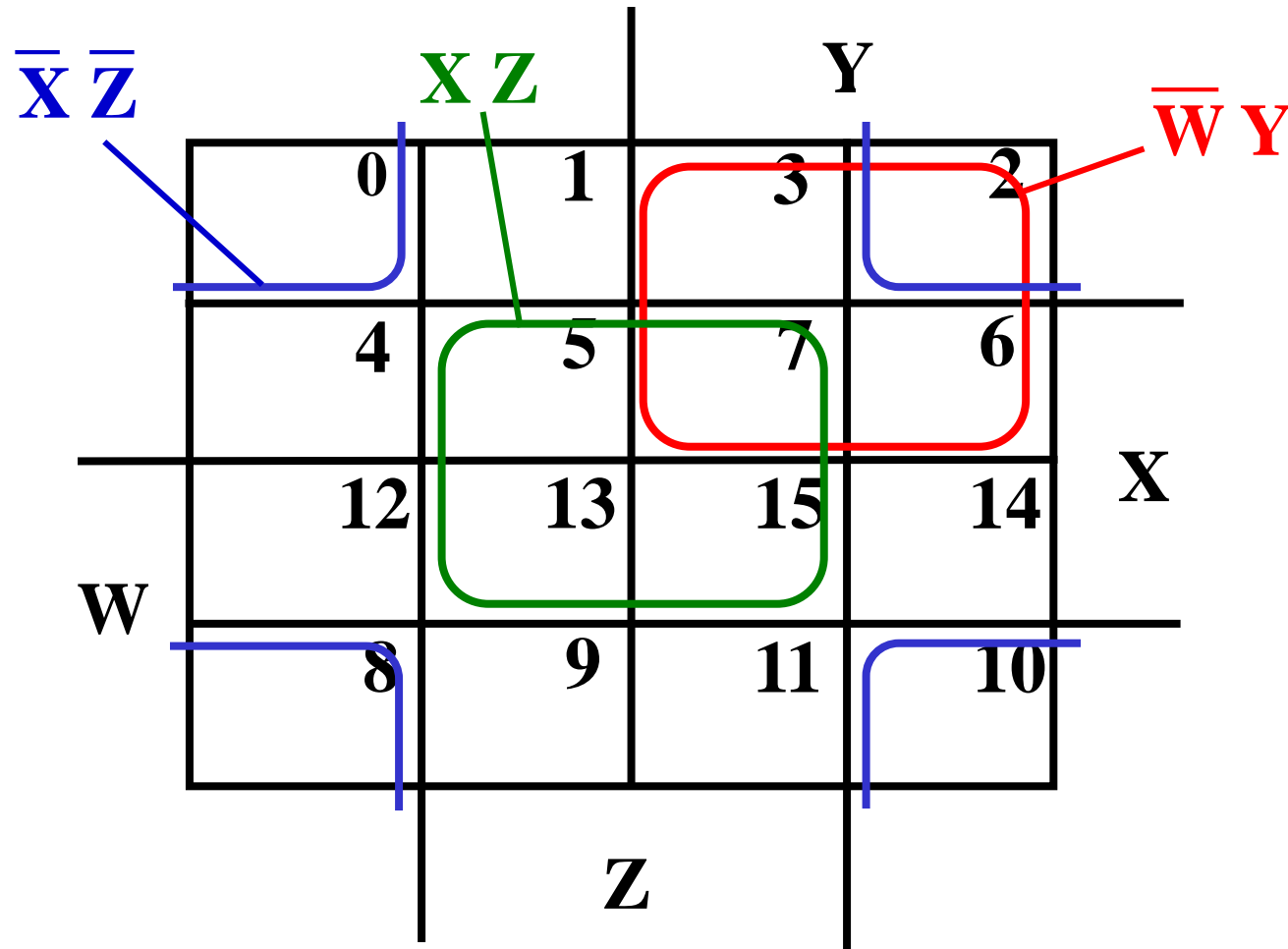


# Combining Two Squares

- Examples of 2-square Rectangles:

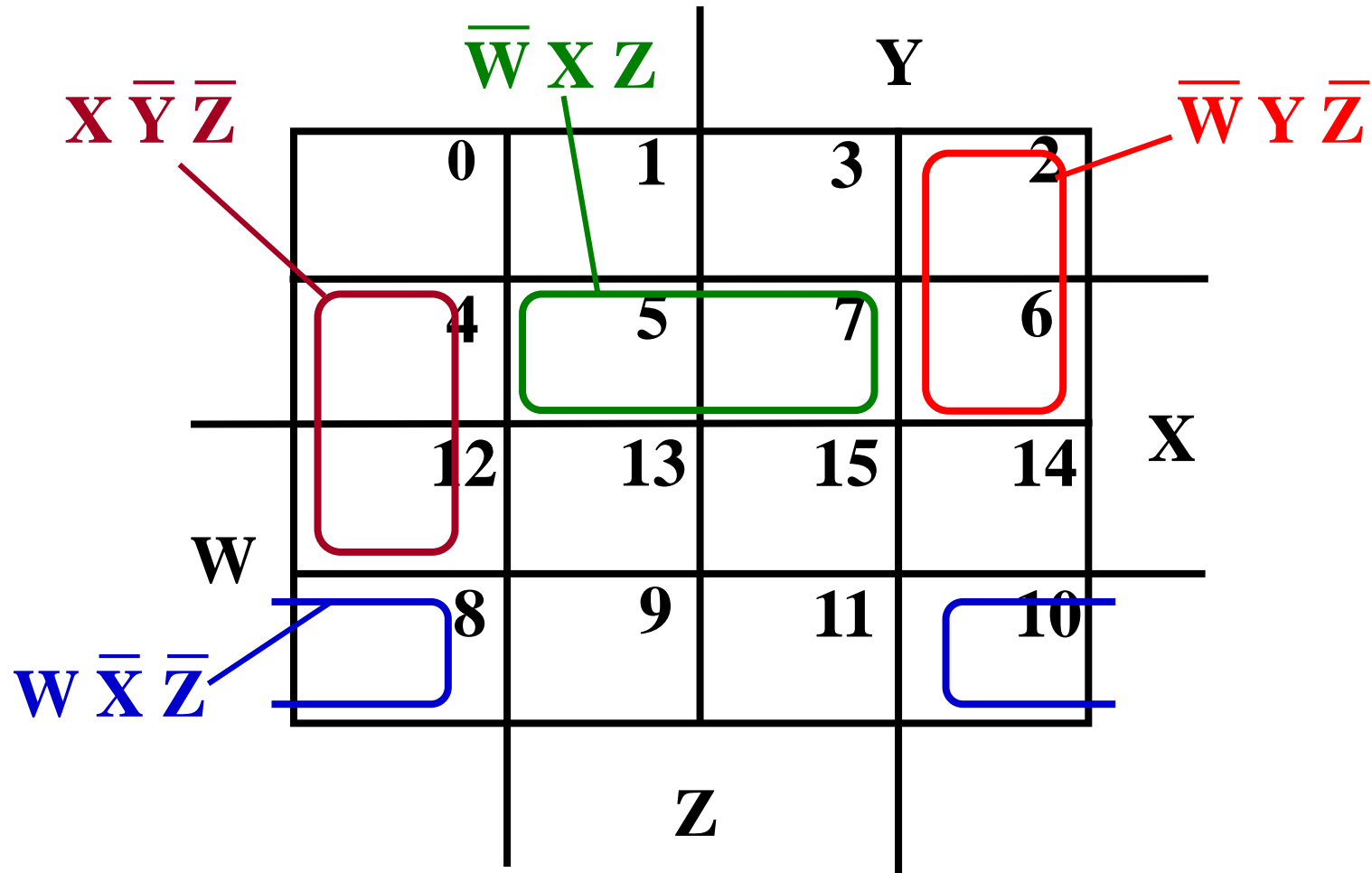
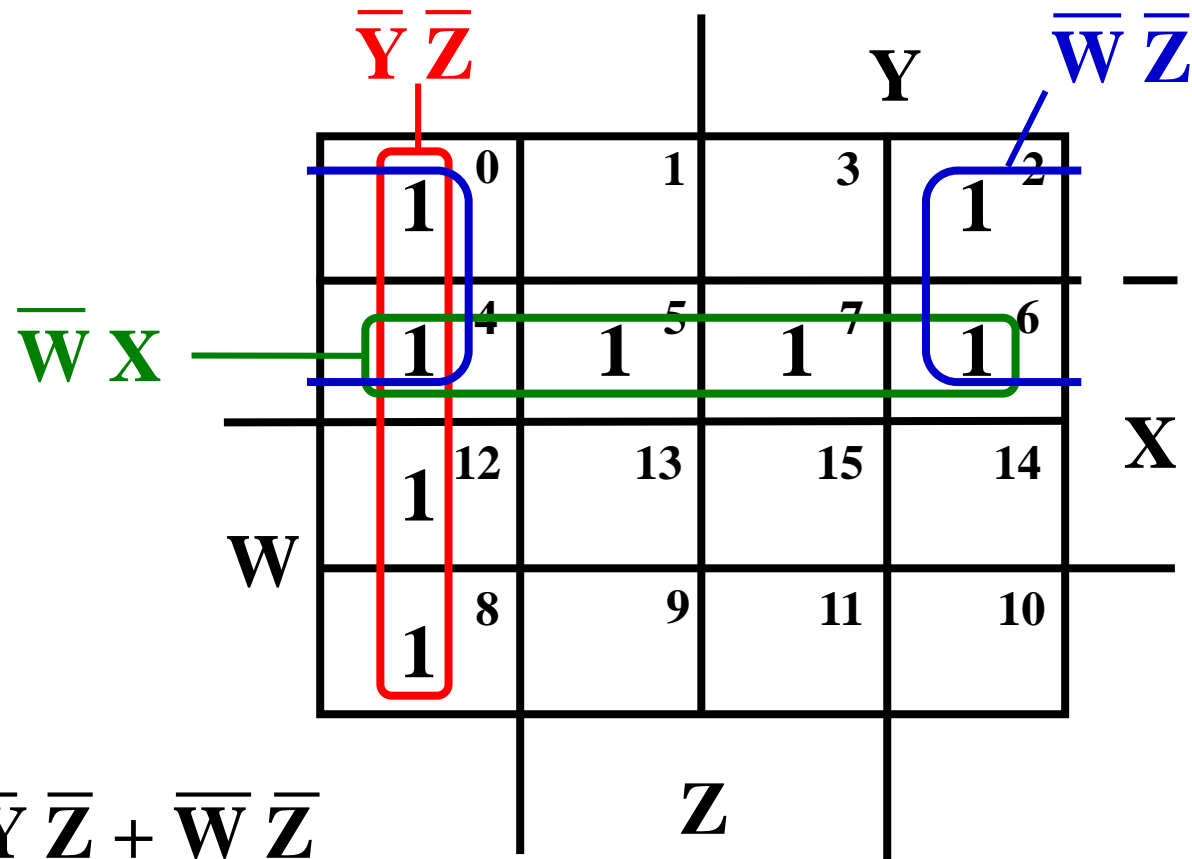
# Simplifying 4-Variable Functions

- $\mathbf{F(W, X, Y, Z)} = \sum (0, 2, 4, 5, 6, 7, 8, 12)$



$$\mathbf{F} = \overline{\mathbf{W}} \mathbf{X} + \overline{\mathbf{Y}} \overline{\mathbf{Z}} + \overline{\mathbf{W}} \overline{\mathbf{Z}}$$

# Product-of-Sums Simplification

---



- Step 1: Draw the K-map for  $\overline{F}$ , replacing the 0's of  $F$  with 1's in  $\overline{F}$  and vice versa
- Step 2: Obtain a minimal Sum-of-Product (SOP) expression for  $\overline{F}$
- Step 3: Use DeMorgan's Theorem to obtain  $F = \overline{\overline{F}}$

The result is a minimal Product-of-Sum (POS) expression for  $F$

- Step 4: Compare the cost of the minimal SOP and POS expressions to find which one is better
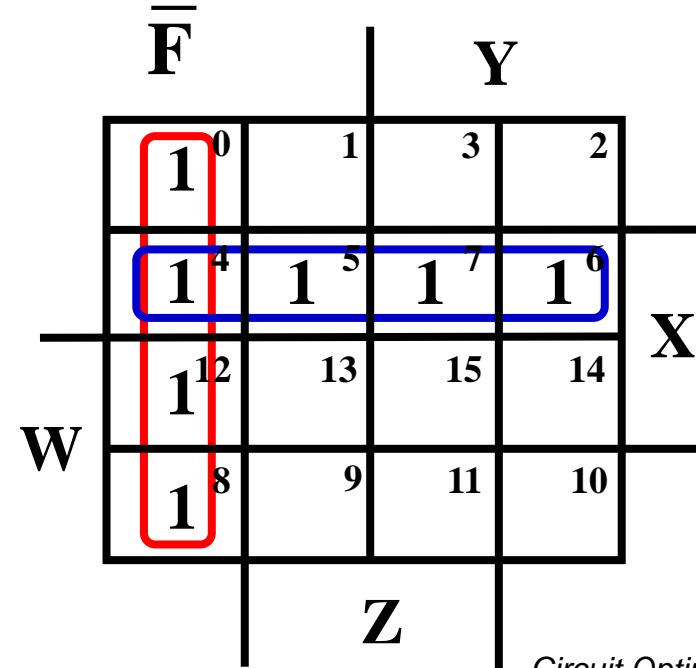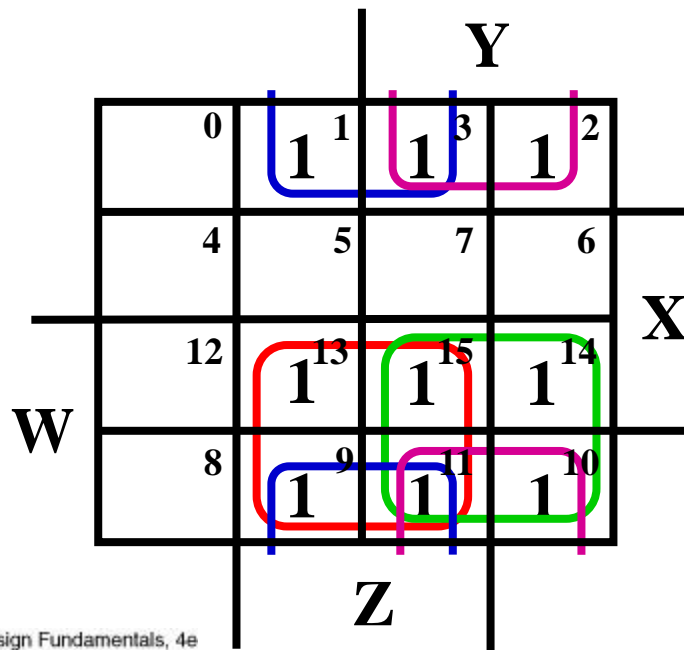
# Product-Of-Sums Simplification

- $F(W, X, Y, Z) = \sum (1, 2, 3, 9, 10, 11, 13, 14, 15)$
- $F = \textcolor{red}{WZ} + \textcolor{green}{WY} + \textcolor{blue}{\bar{X}Z} + \textcolor{magenta}{\bar{X}Y}$  ( $G = 8+4 = 12$ )
- $\bar{F}(W, X, Y, Z) = \sum (0, 4, 5, 6, 7, 8, 12) = \textcolor{red}{\bar{Y}\bar{Z}} + \textcolor{blue}{\bar{W}X}$
- $F = \overline{\bar{Y}\bar{Z} + \bar{W}X} = (Y + Z)(W + \bar{X})$  ( $G = 4+2 = 6$ )



# The End

---

## Questions?