



Computer Science Department



Cairo University

CS504

Digital Logic & Computer Organization

Lecture 5

Lecture Outline (Chapter 3)

- ★ Don't Cares in K-Maps (Section 3.5)
- ★ Other Gate Types (NAND and NOR) (Section 3.6)
 - NAND Gate
 - NAND-NAND Implementation
 - Multi-Level NAND Circuits
 - NOR Gate
 - NOR-NOR Implementation
 - Multi-Level NOR Circuits

Don't Cares in K-Maps

- Sometimes a function table or K-map contains entries for which it is known:
 - The input values for the minterm will never occur, or
 - The output value for the minterm is not used
- In these cases, the output value need not be defined
- Instead, the output value is defined as a **“don't care”**
- By placing “don't cares” (an “x” entry) in the function table or map, the cost of the logic circuit may be lowered.
- Example: A logic function having the binary codes for the BCD digits as its inputs. Only the codes for 0 through 9 are used. The six codes, 1010 through 1111 **never occur**, so the output values for these codes are “x = don't cares.”

Example: BCD “5 or More”

- The map below gives a function $F(w,x,y,z)$ which is defined as "5 or more" over BCD inputs. With the don't cares used for the 6 non-BCD combinations:


- If the don't cares were treated as 0's we get:

$$F1 = \bar{w} x z + \bar{w} x y + w \bar{x} \bar{y} \quad (G = 12)$$

- If the don't cares were 1's we get:

$$F2 = w + x z + x y \quad (G = 7 \text{ better})$$

 The selection of don't cares depends on which combination gives the simplest expression



Product-of-Sums Example

- Find the optimum POS expression for :

$$F(A, B, C, D) = \sum (3, 9, 11, 12, 13, 14, 15) + \sum_d (1, 4, 6)$$

Where \sum_d indicates the don't care minterms


- Solution: Find $\bar{F} = \sum (0, 2, 5, 7, 8, 10) + \sum_d (1, 4, 6)$

- $\bar{F} = \bar{B} \bar{D} + \bar{A} B$

- Optimum POS expression:

$$F = (B + D) (A + \bar{B})$$

Gate input cost ($G = 6$)

 


Systematic Simplification

- A **Prime Implicant** is a product term obtained by combining the **maximum possible number of adjacent squares** in the map into a rectangle, with the number of squares equal to a power of 2.
- A prime implicant is called an **Essential Prime Implicant** if it is the **only** prime implicant that covers one or more minterms.
- Prime Implicants and Essential Prime Implicants can be determined by inspection of a K-Map.
- A set of prime implicants **covers all minterms** if, for each minterm of the function, at least one prime implicant in the set of prime implicants includes the minterm.

Example of Prime Implicants

- Find ALL Prime Implicants

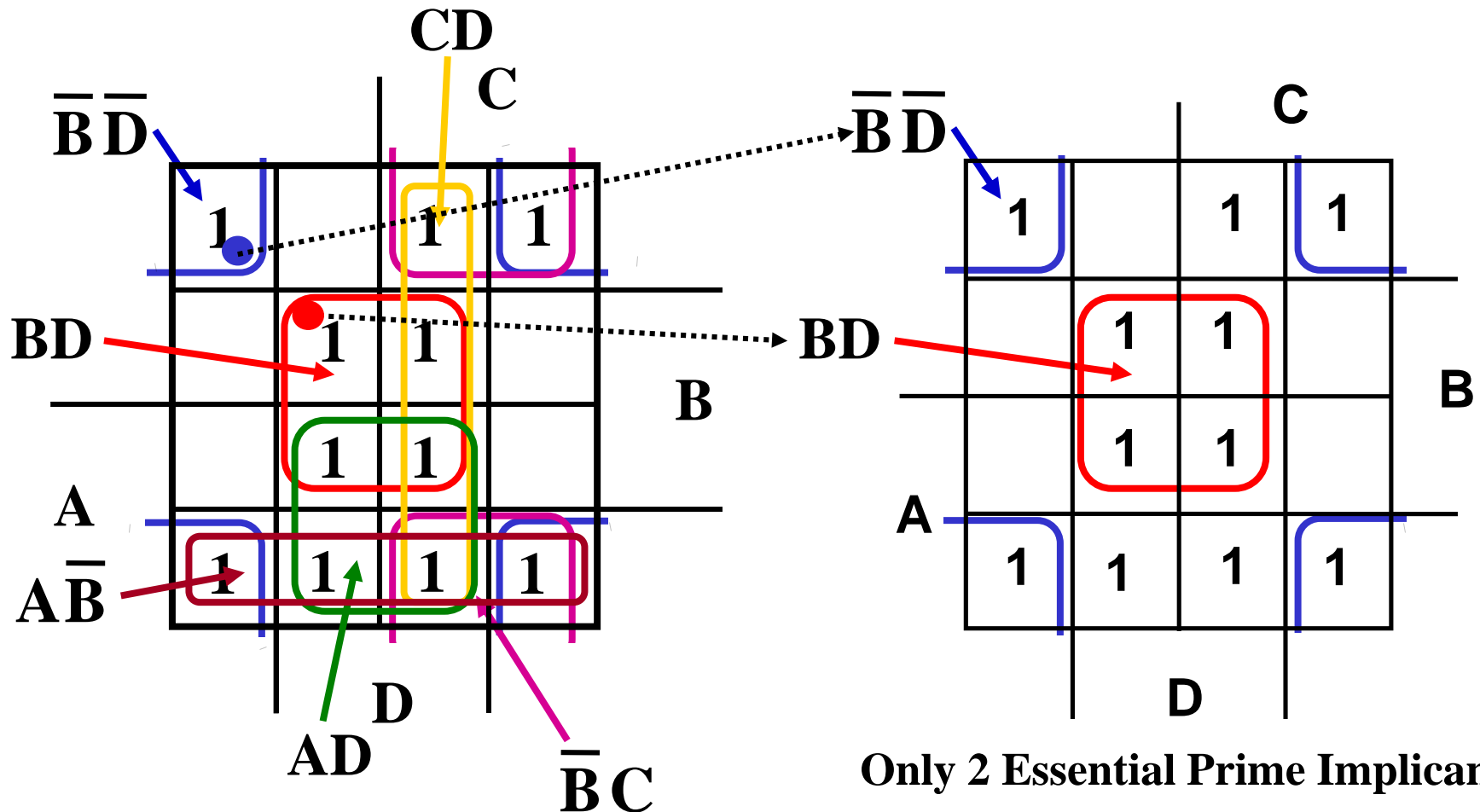

Prime Implicant Practice


- Find all prime implicants for

$$F(A, B, C, D) = \sum (0, 2, 3, 8, 9, 10, 11, 12, 13, 14, 15)$$

3 prime implicants:

A , $\bar{B} C$, $\bar{B} \bar{D}$

All 3 prime implicants are essential

 


Optimization Algorithm

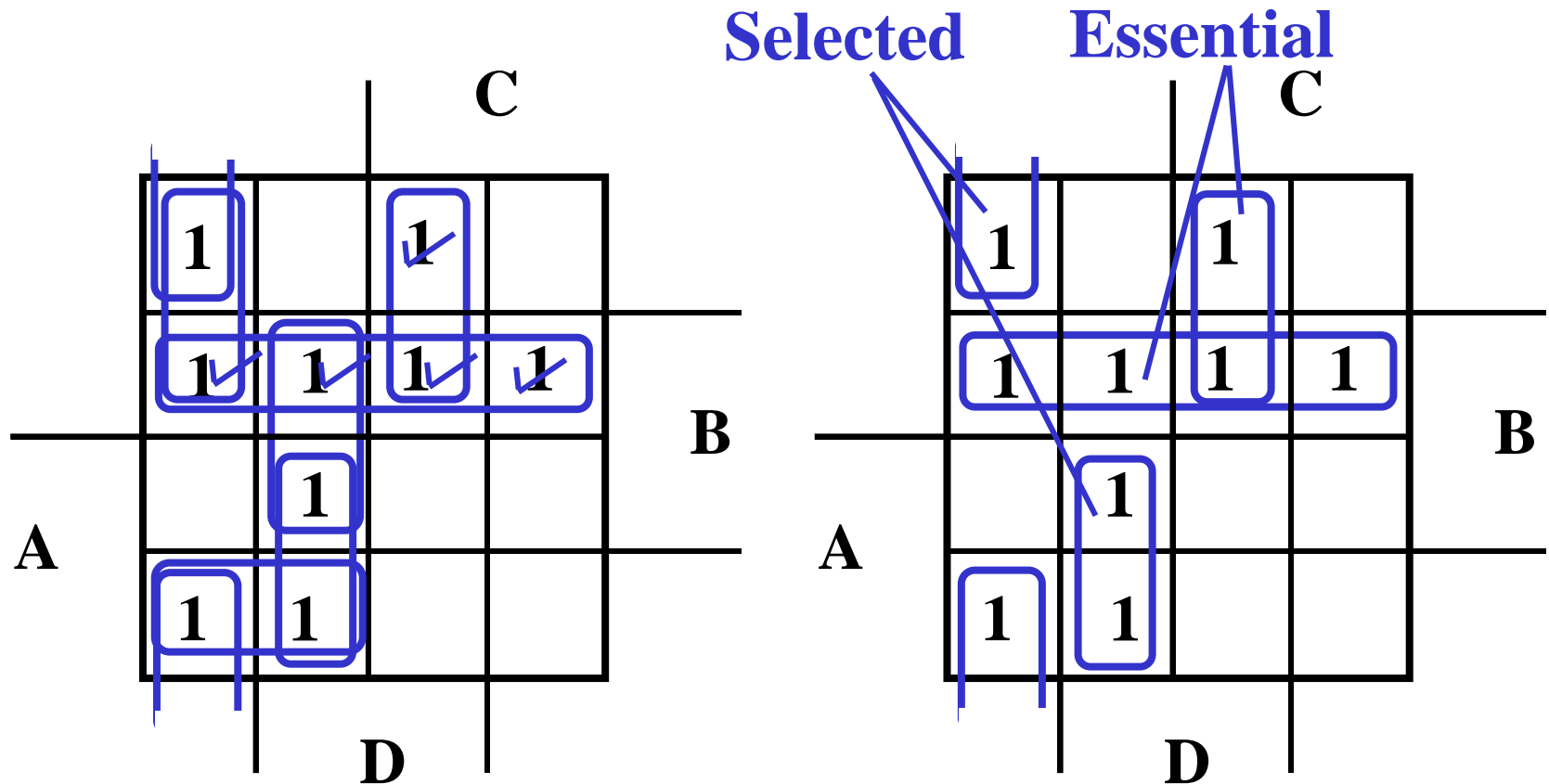1. Find **all** prime implicants.
 2. Include **all essential** prime implicants in the solution.
 3. Select a minimum cost set of non-essential prime implicants to cover all minterms not yet covered.
- Prime implicant selection rule:
 - A. Minimize the overlap among prime implicants.
 - B. In particular, in the final solution, make sure that each prime implicant selected includes at least one minterm not included in any other prime implicant selected.

Selection Rule Example


- Simplify $F(A, B, C, D)$ given on the K-map



✓ Minterms covered by essential prime implicants

Selection Rule Example with Don't Cares

 - Simplify $F(A, B, C, D)$ given on the K-map.



✓ Minterms covered by essential prime implicants

Other Gate Types (NAND and NOR)


- Why?
 - Ease of fabrication
 - Low cost implementation
 - Digital circuits are made of NAND or NOR, rather than AND and OR gates

- We need rules to convert from AND/OR/NOT to NAND/NOR circuits

NAND Gate

- The basic NAND gate has the following symbol and truth table:

- AND-Invert (NAND) Symbol:

 


X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

- NAND represents **NOT AND**. The small “bubble” circle represents the invert function
- The NAND gate is implemented efficiently in **CMOS technology** in terms of chip area and speed

NAND Gate: Invert-OR Symbol

 
- Applying DeMorgan's Law: **Invert-OR = NAND**




- This NAND symbol is called **Invert-OR**
 - Since inputs are inverted and then ORed together
- AND-Invert & Invert-OR both represent NAND gate
 - Having both makes visualization of circuit function easier
- Unlike AND, the NAND operation is **NOT associative**
 $(X \text{ NAND } Y) \text{ NAND } Z \neq X \text{ NAND } (Y \text{ NAND } Z)$

The NAND Gate is Universal

 - NAND gates can implement any Boolean function
- NAND gates can be used as inverters, or to implement AND / OR operations
- A NAND gate with one input is an inverter
- AND is equivalent to NAND with **inverted output**



 - OR is equivalent to NAND with **inverted inputs**






NAND–NAND Implementation

- Consider the Following SOP Expression:

$$F = XZ + \overline{W}Y\overline{Z}$$

   
- A 2-level AND-OR circuit can be converted easily to a **NAND-NAND implementation**




Two successive bubbles
on the same line cancel
each other

NAND–NAND Implementation (2)

 
- Requires function to be in SOP form
- Example: $F = AB + CD = ((AB)' \cdot (CD)')'$
- Three ways to implement F



(a)

 

(b)

 


(c)

Fig. 3-20 Three Ways to Implement $F = AB + CD$


Multilevel NAND Circuits

- SOP results in two-level designs
- Not all designs are two-level, e.g., $F=A(CD+B)+BC'$
- How do we convert multilevel circuits to NAND circuits?
- Rules
 - 1-Convert all ANDs to NAND gates with AND-invert symbol
 - 2-Convert all ORs to NAND gates with invert-OR symbols
 - 3-Check the bubbles, insert bubble if not compensated

Multilevel NAND Circuits (2)

 

(a) AND-OR gates

 


(b) NAND gates

Fig. 3-23 Implementing $F = (AB' + A'B)(C + D')$

NOR Gate

- The basic NOR gate has the following symbol and truth table:

- **OR-Invert (NOR) Symbol:**

 


X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- NOR represents **NOT OR**. The small “bubble” circle represents the invert function.
- The NOR gate is also implemented efficiently in **CMOS technology** in terms of chip area and speed

NOR Gate: Invert-AND Symbol

 
- The **Invert-AND** symbol is also used for **NOR**




- This NOR symbol is called **Invert-AND**, since inputs are inverted and then ANDed together
- OR-Invert & Invert-AND both represent NOR gate
 - Having both makes visualization of circuit function easier
- Unlike OR, the NOR operation is **NOT associative**
 $(X \text{ NOR } Y) \text{ NOR } Z \neq X \text{ NOR } (Y \text{ NOR } Z)$

The NOR Gate is also Universal

 - NOR gates can implement any Boolean function
- NOR gates can be used as inverters, or to implement AND / OR operations
- A NOR gate with one input is an inverter
- OR is equivalent to NOR with **inverted output**



 - AND is equivalent to NOR with **inverted inputs**





NOR–NOR Implementation


- Consider the Following POS Expression:

$$F = (X + \bar{Z})(W + \bar{Y} + Z)$$

  - A 2-level OR-AND circuit can be converted easily to a **NOR-NOR implementation**



 Two successive bubbles
on the same line cancel
each other



NOR–NOR Implementation (2)

- Requires function to be in POS form
- Example: $F = (A+B) \cdot (C+D) \cdot E$
- $F = ((A+B)' + (C+D)' + E')'$

 


Fig. 3-26 Implementing $F = (A + B)(C + D)E$

Multilevel NOR Circuits

- POS results in two-level designs
- Not all designs are two-level, e.g., $F=(AB'+A'B)(C+D')$
- How do we convert multilevel circuits to NOR circuits?
- Rules

1-Convert all ORs to NOR gates with OR-invert symbol

2-Convert all ANDs to NOR gates with invert-AND symbols

3-Check the bubbles, insert bubble if not compensated

Multilevel NOR Circuits (2)



 


Fig. 3-27 Implementing $F = (AB' + A'B)(C + D')$ with NOR Gates


Multilevel NOR Circuits (3)

 

(a) AND-OR diagram

 

(b) NOR diagram

 

(c) Alternate NOR diagram

The End

Questions?